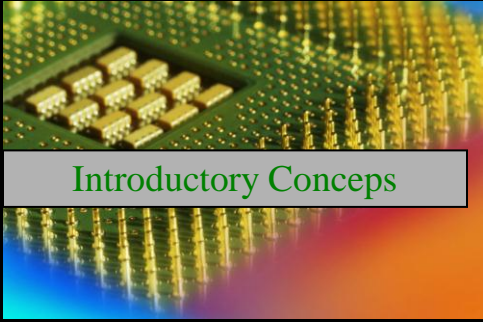


EEE251 Logic Design and Circuits

Assist.Prof. Yavuz BAYAM




Introductory Concepts

October 1, 2012

Introductory

Analog Quantities

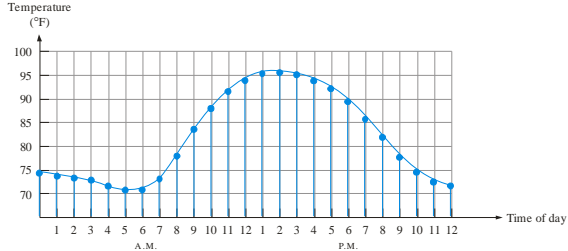Most natural quantities that we see are **analog** and vary continuously. Analog systems can generally handle higher power than digital systems.



| Time of day | Temperature (°F) |
|-------------|------------------|
| 1 A.M. | 75 |
| 2 A.M. | 74 |
| 3 A.M. | 73 |
| 4 A.M. | 72 |
| 5 A.M. | 72 |
| 6 A.M. | 72 |
| 7 A.M. | 75 |
| 8 A.M. | 80 |
| 9 A.M. | 85 |
| 10 A.M. | 90 |
| 11 A.M. | 93 |
| 12 P.M. | 95 |
| 1 P.M. | 95 |
| 2 P.M. | 95 |
| 3 P.M. | 94 |
| 4 P.M. | 92 |
| 5 P.M. | 90 |
| 6 P.M. | 85 |
| 7 P.M. | 80 |
| 8 P.M. | 78 |
| 9 P.M. | 76 |
| 10 P.M. | 75 |
| 11 P.M. | 74 |
| 12 P.M. | 73 |


Digital systems can process, store, and transmit data more efficiently but can only assign discrete values to each point.

Floyd, Digital Fundamentals, 10th ed
© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Analog and Digital Systems

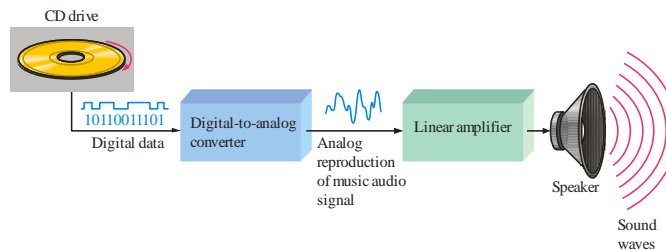- Many systems use a mix of analog and digital electronics to take advantage of each technology.
- A typical CD player accepts digital data from the CD drive and converts it to an analog signal for amplification.



Floyd, Digital Fundamentals, 10th ed


© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Binary Digits and Logic Levels

- Digital electronics uses circuits that have two states, which are represented by two different voltage levels called HIGH and LOW.
- The voltages represent numbers in the binary system.

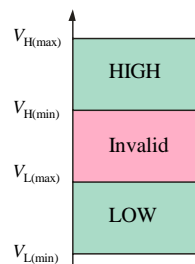In binary, a single number is called a *bit* (for *binary digit*). A bit can have the value of either a 0 or a 1, depending on if the voltage is HIGH or LOW.




Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved


Summary

Digital Waveforms

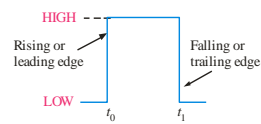- Digital waveforms change between the LOW and HIGH levels.
- A positive going pulse is one that goes from a normally LOW logic level to a HIGH level and then back again.
- Digital waveforms are made up of a series of pulses.



(a) Positive-going pulse

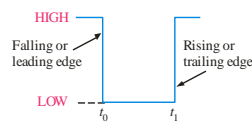

(b) Negative-going pulse


Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Pulse Definitions

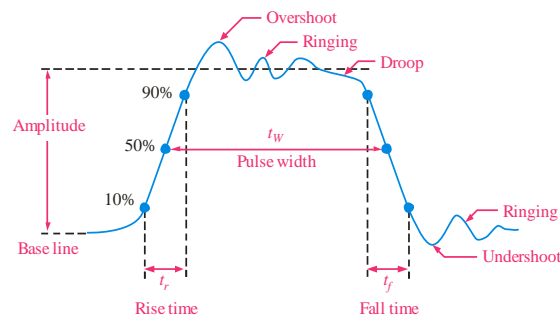Actual pulses are not ideal but are described by the rise time, fall time, amplitude, and other characteristics.



Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Periodic Pulse Waveforms

Periodic pulse waveforms are composed of pulses that repeats in a fixed interval called the **period**.

The **frequency** is the rate it repeats and is measured in hertz.

$$f = \frac{1}{T} \quad T = \frac{1}{f}$$

The **clock** is a basic timing signal that is an example of a periodic wave.


Example What is the period of a repetitive wave if $f = 3.2 \text{ GHz}$?

Solution $T = \frac{1}{f} = \frac{1}{3.2 \text{ GHz}} = 313 \text{ ps}$

Summary

Pulse Definitions

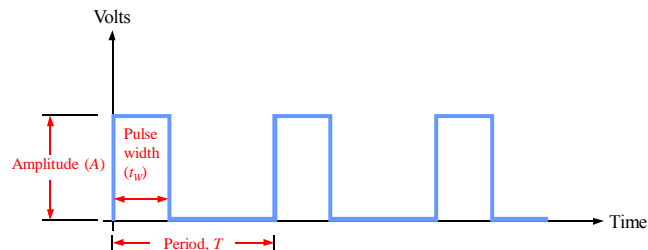In addition to frequency and period, repetitive pulse waveforms are described by the amplitude (A), pulse width (t_W) and duty cycle. Duty cycle is the ratio of t_W to T .




Summary

Example

For the periodic digital wave form below determine the following;

- a) Period b) frequency c) duty cycle

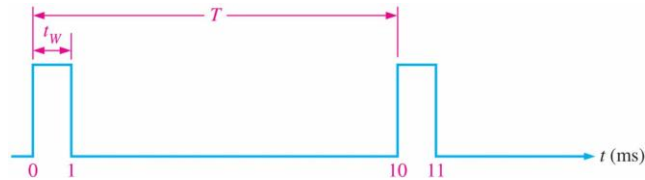

Solution:


Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Timing Diagrams

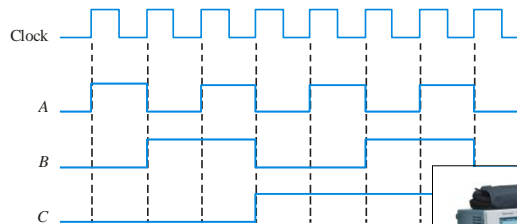A timing diagram is used to show the relationship between two or more digital waveforms,



A diagram like this can be observed directly on a logic analyzer.




Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Serial and Parallel Data

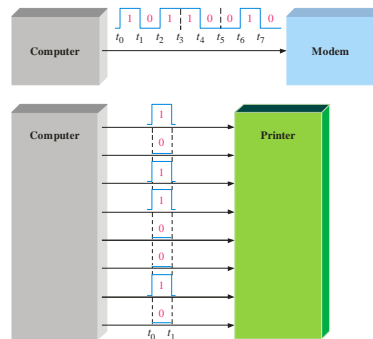Data can be transmitted by either serial transfer or parallel transfer.



Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Basic Logic Functions

AND

True only if **all** input conditions are true.



OR

True only if **one or more** input conditions are true.



NOT

Indicates the **opposite** condition.




Floyd, Digital Fundamentals, 10th ed


© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

And Gate

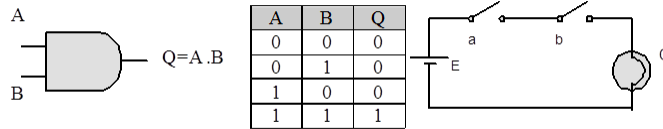


Or Gate

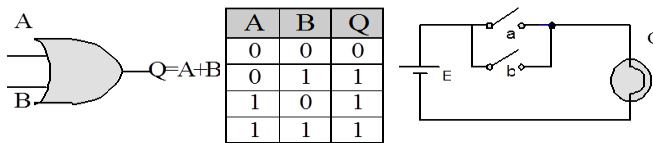Floyd, Digital Fundamentals, 10th ed


© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

And Gate

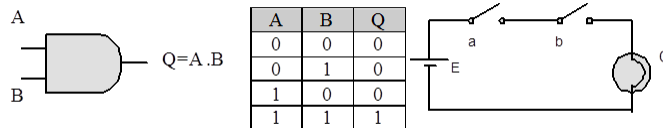

Or Gate

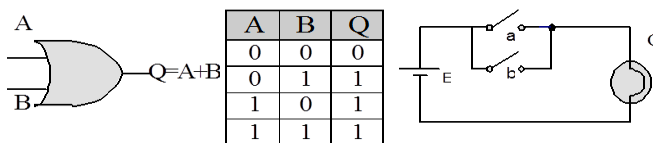Floyd, Digital Fundamentals, 10th ed


© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary


Basic System Functions

And, **or**, and **not** elements can be combined to form various logic functions. A few examples are:

The comparison function

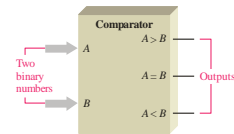

Basic arithmetic functions

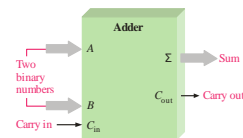


Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved


Summary

Basic System Functions

The encoding function

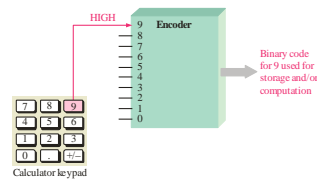

The decoding function

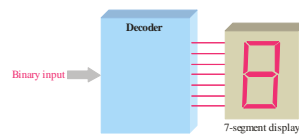


Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Basic System Functions

The data selection function

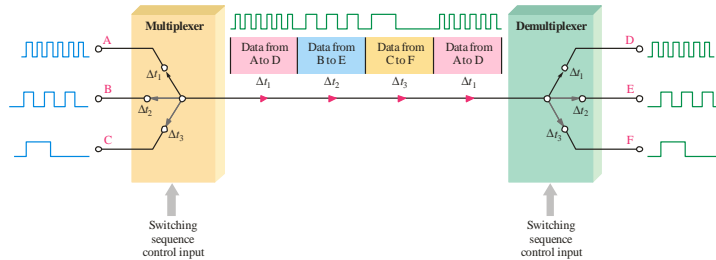
Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Basic System Functions

The counting function

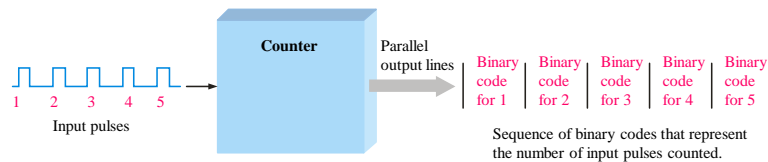

...and other functions such as code conversion and storage.


Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary

Basic System Functions

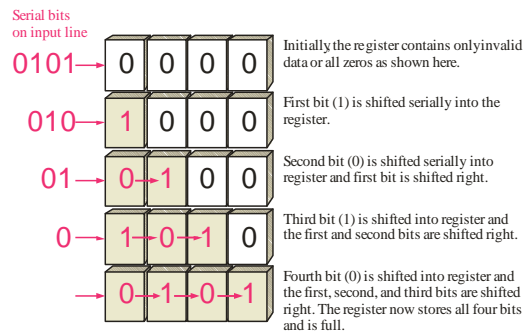
One type of storage function is the shift register, that moves and stores data each time it is clocked.



Summary

Integrated Circuits

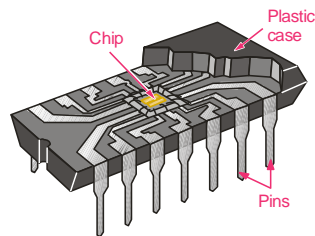Cutaway view of DIP (Dual-In-line Pins) chip:



The TTL series, available as DIPs are popular for laboratory experiments with logic.

Summary

Integrated Circuits

An example of laboratory prototyping is shown. The circuit is wired using DIP chips and tested.


In this case, testing can be done by a computer connected to the system.



Summary

Integrated Circuits


DIP chips and surface mount chips

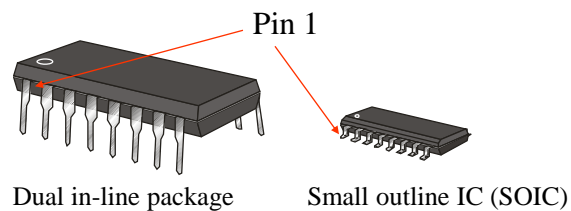

Summary

Integrated Circuits

Other surface mount packages:

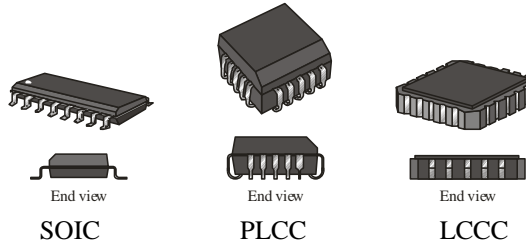

Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Summary


Test and Measurement Instruments

The DMM can make three basic electrical measurements.

Voltage

Resistance

Current

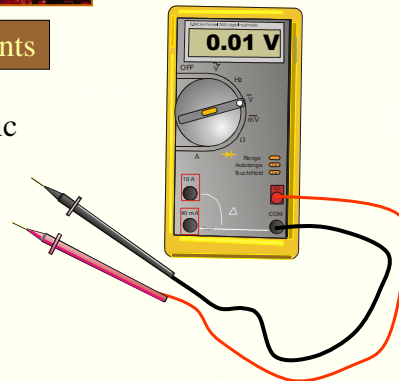

In digital work, DMMs are useful for checking power supply voltages, verifying resistors, testing continuity, and occasionally making other measurements.

Floyd, Digital Fundamentals, 10th ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Selected Key Terms

- Analog** Being continuous or having continuous values.
- Digital** Related to digits or discrete quantities; having a set of discrete values.
- Binary** Having two values or states; describes a number system that has a base of two and utilizes 1 and 0 as its digits.
- Bit** A binary digit, which can be a 1 or a 0.
- Pulse** A sudden change from one level to another, followed after a time, called the pulse width, by a sudden change back to the original level.

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Selected Key Terms

- Clock** A basic timing signal in a digital system; a periodic waveform used to synchronize actions.
- Gate** A logic circuit that performs a basic logic operations such as AND or OR.
- NOT** A basic logic function that performs inversion.
- AND** A basic logic operation in which a true (HIGH) output occurs only when all input conditions are true (HIGH).
- OR** A basic logic operation in which a true (HIGH) output occurs when when one or more of the input conditions are true (HIGH).

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Selected Key Terms

- Fixed-function logic*** A category of digital integrated circuits having functions that cannot be altered.
- Programmable logic*** A category of digital integrated circuits capable of being programmed to perform specified functions.

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Quiz

1. Compared to analog systems, digital systems
 - a. are less prone to noise
 - b. can represent an infinite number of values
 - c. can handle much higher power
 - d. all of the above

© 2008 Pearson Education

Quiz

2. The number of values that can be assigned to a bit are
- a. one
 - b. two
 - c. three
 - d. ten

© 2008 Pearson Education

Quiz

3. The time measurement between the 50% point on the leading edge of a pulse to the 50% point on the trailing edge of the pulse is called the
- a. rise time
 - b. fall time
 - c. period
 - d. pulse width

© 2008 Pearson Education

Quiz

4. The time measurement between the 90% point on the trailing edge of a pulse to the 10% point on the trailing edge of the pulse is called the

- a. rise time
- b. fall time
- c. period
- d. pulse width

© 2008 Pearson Education

Quiz

5. The reciprocal of the frequency of a clock signal is the

- a. rise time
- b. fall time
- c. period
- d. pulse width

© 2008 Pearson Education

Quiz

6. If the period of a clock signal is 500 ps, the frequency is
- a. 20 MHz
 - b. 200 MHz
 - c. 2 GHz
 - d. 20 GHz

© 2008 Pearson Education

Quiz

7. AND, OR, and NOT gates can be used to form
- a. storage devices
 - b. comparators
 - c. data selectors
 - d. all of the above

© 2008 Pearson Education

Quiz

8. A shift register is an example of a
- a. storage device
 - b. comparator
 - c. data selector
 - d. counter

© 2008 Pearson Education

Quiz

9. A device that is used to switch one of several input lines to a single output line is called a
- a. comparator
 - b. decoder
 - c. counter
 - d. multiplexer

© 2008 Pearson Education

Quiz

Answers:

- | | |
|------|-------|
| 1. a | 6. c |
| 2. b | 7. d |
| 3. d | 8. a |
| 4. b | 9. d |
| 5. c | 10. b |

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved